

①

$$C = 10 \mu\text{F} = 10 \cdot 10^{-6} \text{F}$$

$$Q = 40 \mu\text{C} = 40 \cdot 10^{-6} \text{C}$$

$$\text{then } \Delta V = \frac{Q}{C} = \frac{40 \cdot 10^{-6}}{10 \cdot 10^{-6}} = \underline{\underline{4 \text{V}}}$$

②

$$(a) \quad C_{eq} = C_1 + C_2 + C_3 = 10 + 20 + 40 = \underline{\underline{70 \mu\text{F}}}$$

$$(b) \quad \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{10} + \frac{1}{20} + \frac{1}{40} = 0.175 \Rightarrow \underline{\underline{C_{eq} = 5.7 \mu\text{F}}}$$

③

$$U = \frac{C \Delta V^2}{2} \quad \text{then} \quad 20 = \frac{5 \cdot 10^{-6} \cdot \Delta V^2}{2} \Rightarrow \Delta V = \sqrt{\frac{2 \cdot 20}{5 \cdot 10^{-6}}} = \underline{\underline{2828 \text{V}}}$$

④

$$V = k_e \frac{Q}{R} \Rightarrow Q = \frac{VR}{k_e} = \frac{100 \cdot 0.02}{9 \cdot 10^9} = 0.2 \cdot 10^{-9} \text{C} = \underline{\underline{0.2 \text{nC}}}$$

⑤



$$A = a^2 = (0.01)^2 = 10^{-4} \text{m}^2$$


$$h = 0.2 \text{mm} = 0.2 \cdot 10^{-3} \text{m}$$

$$(a) \quad C = \frac{\epsilon_0 A}{h} = \frac{8.85 \cdot 10^{-12} \cdot 10^{-4}}{0.2 \cdot 10^{-3}} = \underline{\underline{0.44 \cdot 10^{-11} \text{F}}}$$



$$(b) \quad Q = C \cdot \Delta V = 0.44 \cdot 10^{-11} \cdot 30 = \underline{\underline{13.2 \cdot 10^{-11} \text{C}}}$$

$$Q_1 = 13.2 \cdot 10^{-11} \text{C}, \quad Q_2 = -13.2 \cdot 10^{-11} \text{C}$$


6

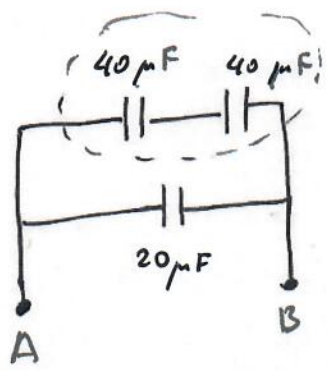
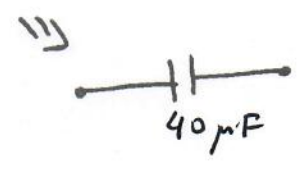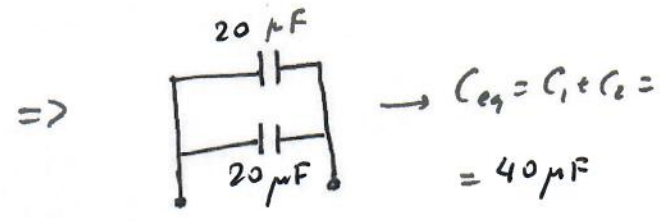
$$\frac{1}{C_{eq}} = \frac{1}{40} + \frac{1}{40} \Rightarrow C_{eq} = 20 \mu F$$





7

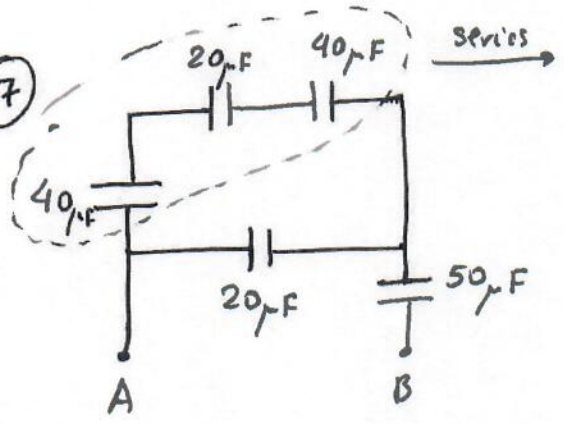

series

$$\frac{1}{C_{eq}^{(1)}} = \frac{1}{40} + \frac{1}{20} + \frac{1}{40} = \frac{4}{40} = \frac{1}{10}$$

$$C_{eq}^{(1)} = 10 \mu F$$

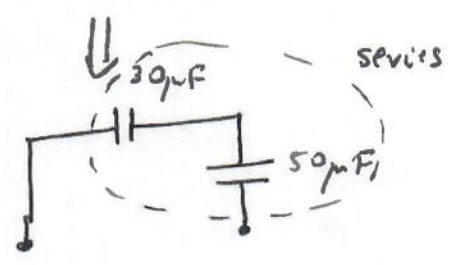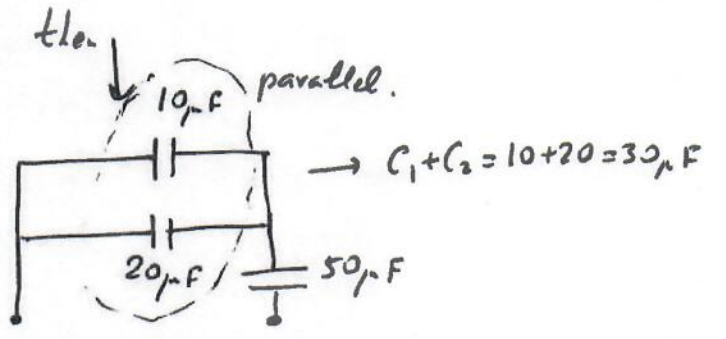

$$\frac{1}{C_{eq}} = \frac{1}{30} + \frac{1}{50} = 0.053$$

$$C_{eq} = 18.75 \mu F$$