

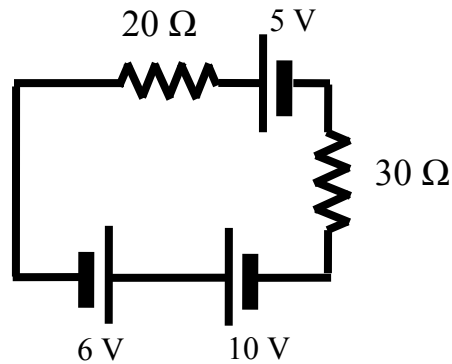
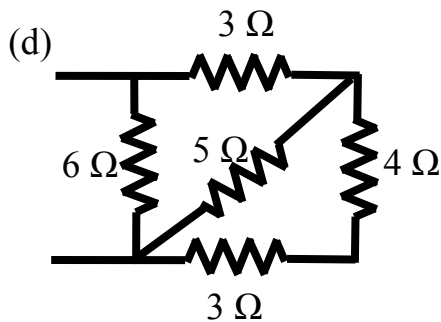


Physics 2212
Homework 5 (due: March 26)


- The electric field inside a 40-cm-long copper wire is 0.050 V/m. (a) What is the potential difference between the ends of the wire? (b) What is the current in the wire? The diameter of the wire is 1 mm.
- A 50-cm-long gold wire is connected across the terminal of a 20 V battery. If the current in the wire is 1.0 A, what is the wire's diameter?
- What is the magnitude and the direction of the current through 20 Ohm resistor shown in the figure?

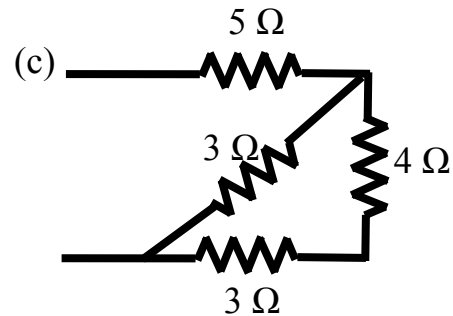

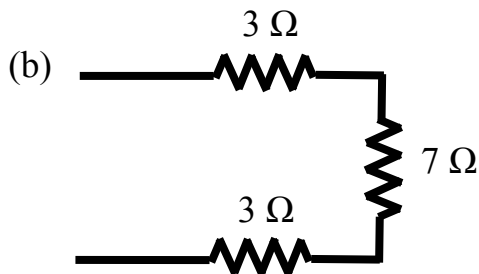
- What is the equivalent resistance of each group of resistors shown in the figure?



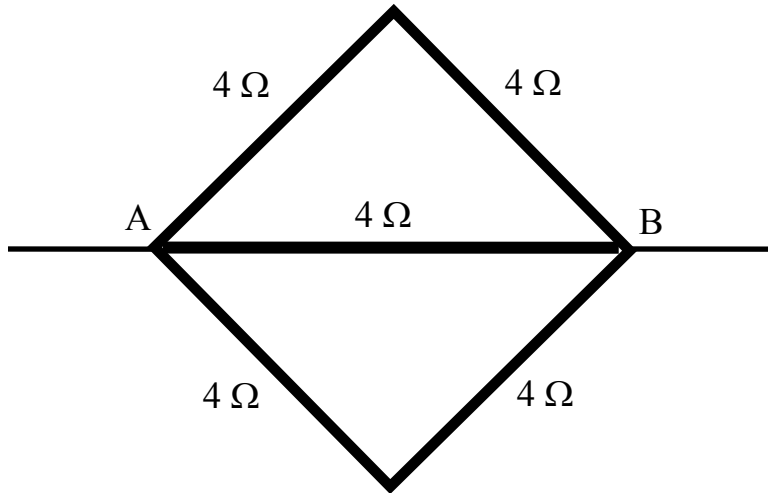
5. Find an equivalent resistance between points A and B.



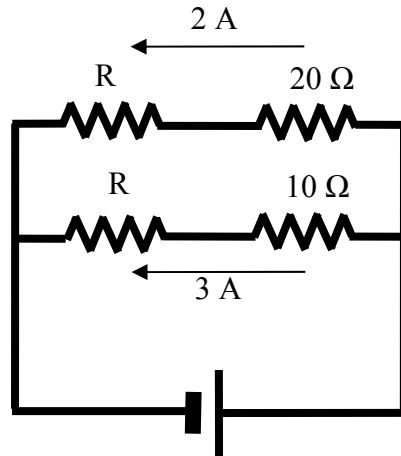
6. What are the resistance R and the emf of the battery in the figure?



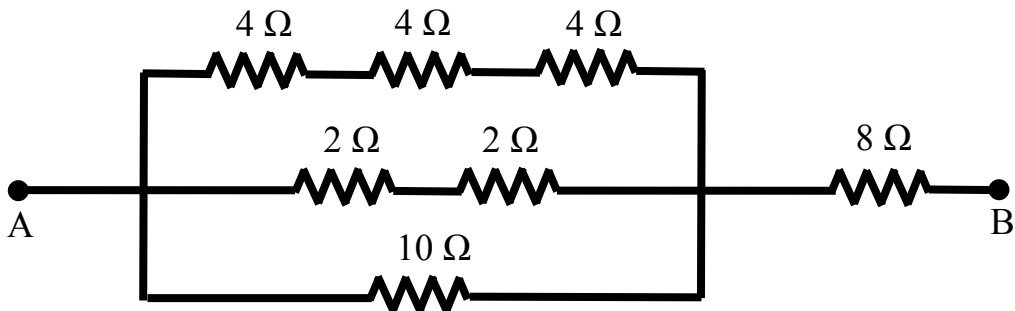
7. What is the equivalent resistance between points A and B?



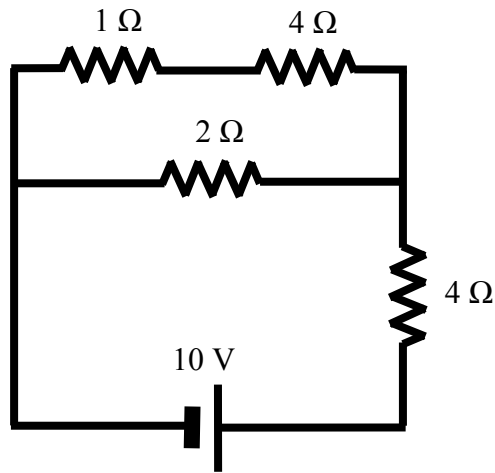8. Find the power delivered to 2 Ohm resistor.



9. Find the current in the circuit.

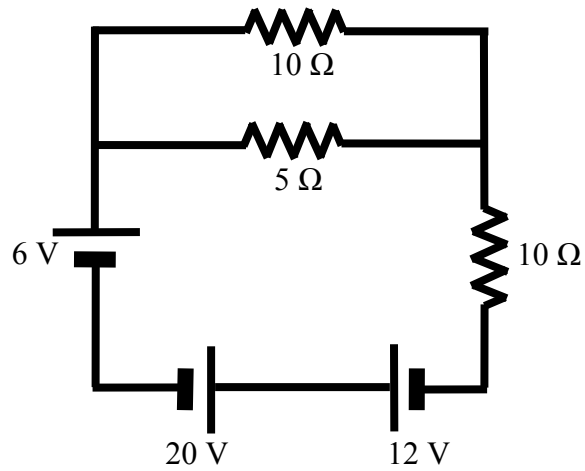

10. Find the current through resistor "1".

