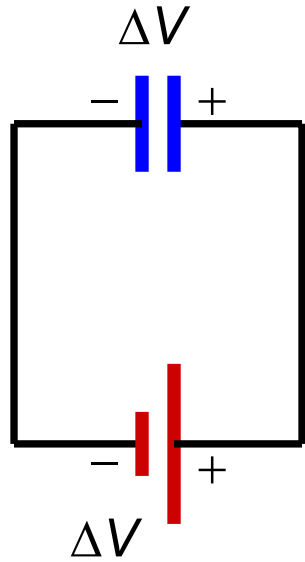


# Chapter 33

## Alternating Current Circuits


# Capacitor




$$Q = C\Delta V$$

# Resistor

$$\Delta V = IR$$

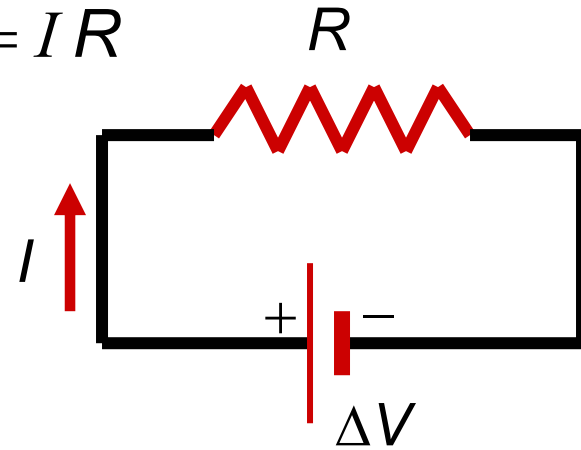

# Inductance

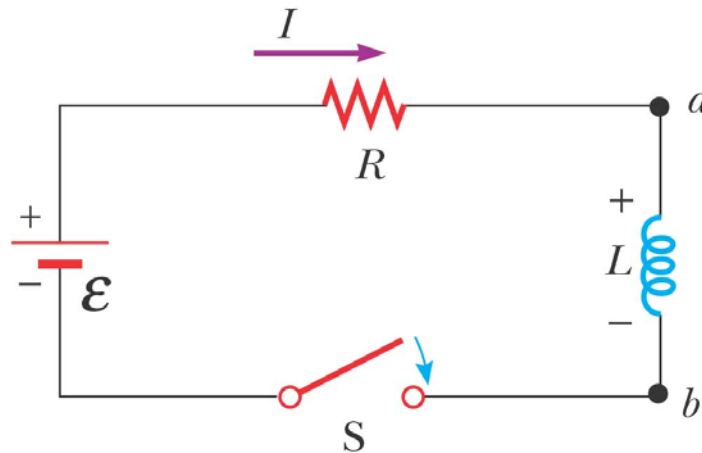

$$\Delta V_{ab} = -L \frac{dI}{dt}$$

# AC power source

- The AC power source provides an alternative voltage,  $\Delta v(t)$
- Notation
  - Lower case symbols will indicate instantaneous values
  - Capital letters will indicate fixed values

- The output of an AC power source is sinusoidal

$$\Delta v = \Delta V_{\max} \sin \omega t$$

- $\Delta v$  is the instantaneous voltage
- $\Delta V_{\max}$  is the maximum output voltage of the source
- $\omega$  is the angular frequency of the AC voltage


# AC voltage

$$\Delta v = \Delta V_{max} \cos(\omega t + \varphi)$$

- The angular frequency is

$$\omega = 2\pi f = \frac{2\pi}{T}$$

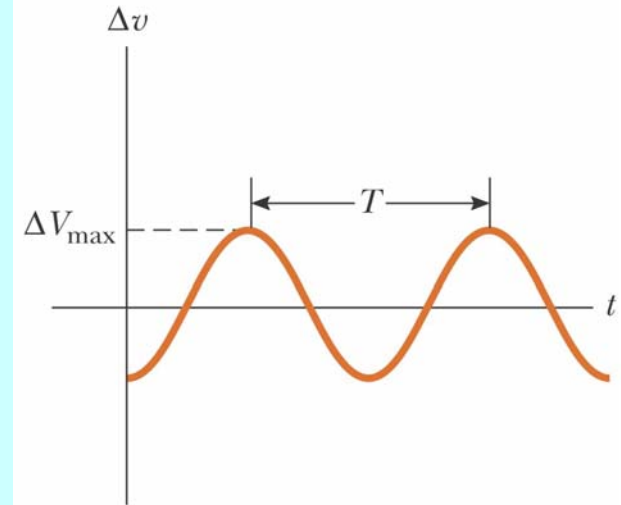- $f$  is the frequency of the source
- $T$  is the period of the source
- The voltage is positive during one half of the cycle and negative during the other half
- The current in any circuit driven by an AC source is an alternating current that varies sinusoidally with time
- Commercial electric power plants in the US use a frequency of 60 Hz



©2004 Thomson - Brooks/Cole


# Resistor in AC circuit

- Consider a circuit consisting of an AC source and a resistor
- The AC source is symbolized by



- $\Delta v = \Delta v_R = \Delta V_{\max} \sin \omega t$
- $\Delta v_R$  is the instantaneous voltage across the resistor
- The instantaneous current in the resistor is
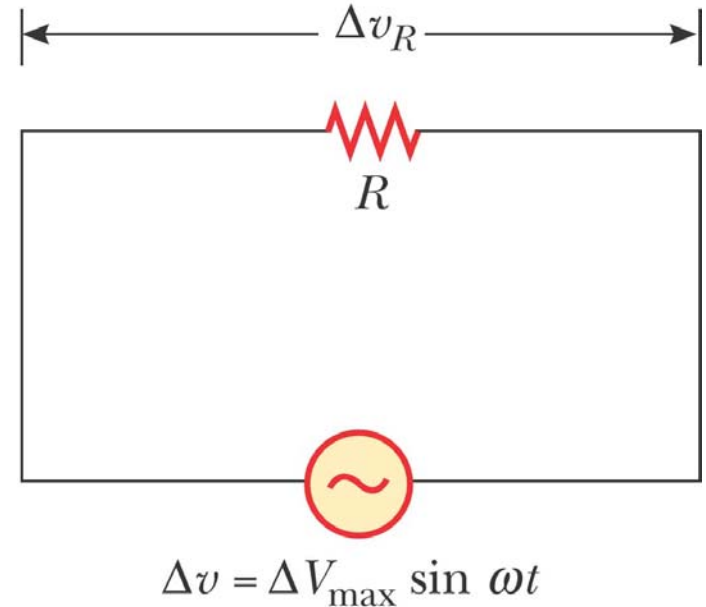
$$i_R = \frac{\Delta v_R}{R} = \frac{\Delta V_{\max}}{R} \sin \omega t = I_{\max} \sin \omega t$$




©2004 Thomson - Brooks/Cole
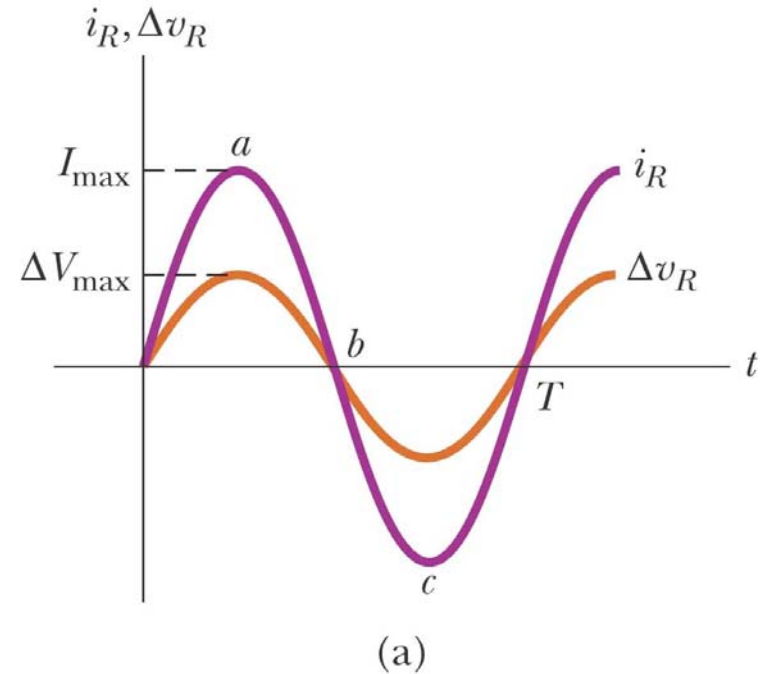
# Resistor in AC circuit

$$\Delta V = \Delta V_R = \Delta V_{max} \sin(\omega t)$$

$$i_R = \frac{\Delta V_R}{R} = \frac{\Delta V_{max}}{R} \sin \omega t = I_{max} \sin \omega t$$




©2004 Thomson - Brooks/Cole

- The current and the voltage are **in phase**
- Resistors behave essentially the same way in both DC and AC circuits
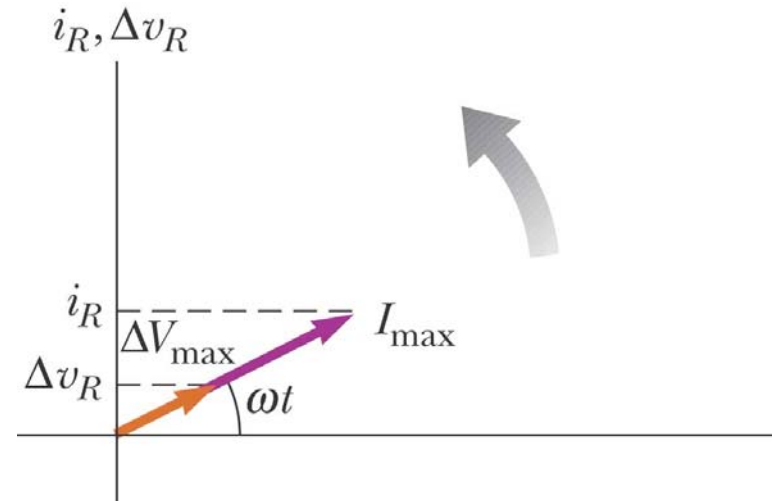
# Resistor in AC circuit: Phasor diagram

$$\Delta V = \Delta V_R = \Delta V_{max} \sin(\omega t)$$

$$i_R = \frac{\Delta V_R}{R} = \frac{\Delta V_{max}}{R} \sin \omega t = I_{max} \sin \omega t$$



- A **phasor** is a vector whose length is proportional to the maximum value of the variable it represents
- The vector rotates at an angular speed equal to the angular frequency associated with the variable
- The projection of the phasor onto the vertical axis represents the instantaneous value of the quantity it represents

# rms current and voltage


$$i_R = I_{max} \sin \omega t$$

- The average current in one cycle is zero
- **rms** stands for **root mean square**

$$\begin{aligned} I_{rms} &= \left( \frac{1}{T} \int_0^T i_R^2 dt \right)^{1/2} = \left( \frac{1}{T} I_{max}^2 \int_0^T \sin^2(\omega t) dt \right)^{1/2} \\ &= \left( \frac{1}{2\pi} I_{max}^2 \int_0^{2\pi} \sin^2(\tau) d\tau \right)^{1/2} = \frac{I_{max}}{\sqrt{2}} = 0.707 I_{max} \end{aligned}$$

- Alternating voltages can also be discussed in terms of rms values
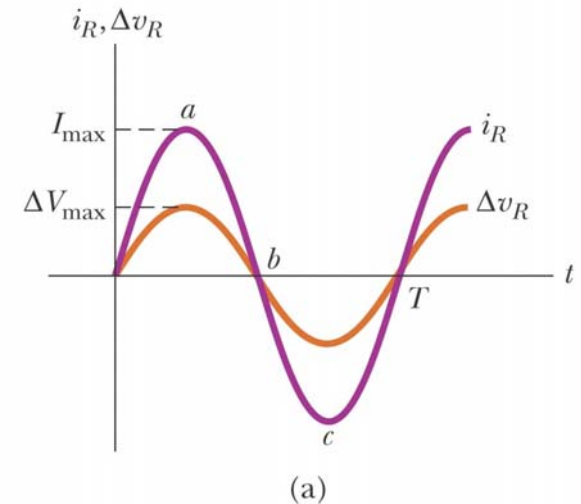
$$\Delta V_{rms} = \frac{\Delta V_{max}}{\sqrt{2}} = 0.707 \Delta V_{max}$$



©2004 Thomson - Brooks/Cole



## rms current and voltage: power

- The rate at which electrical energy is dissipated in the circuit is given by

$$P = i^2 R$$

- where  $i$  is the *instantaneous current*
- The average power delivered to a resistor that carries an alternating current is


$$P_{av} = I_{rms}^2 R$$

# Inductors in AC circuit

$$\Delta v + \Delta v_L = 0, \text{ or}$$

$$\Delta v - L \frac{di}{dt} = 0$$
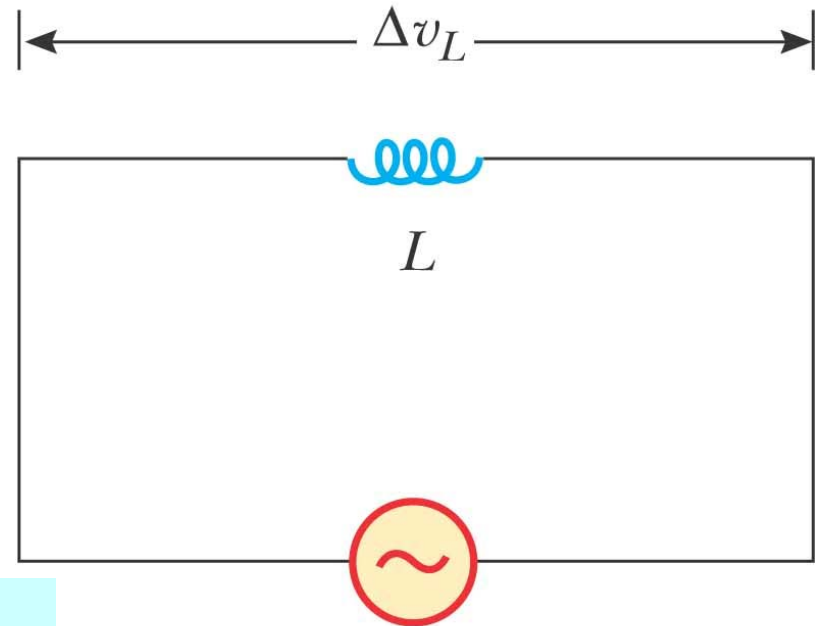
$$\Delta v = L \frac{di}{dt} = \Delta V_{max} \sin \omega t$$



$$i_L = \frac{\Delta V_{max}}{L} \int \sin \omega t \, dt = -\frac{\Delta V_{max}}{\omega L} \cos \omega t$$

$$i_L = \frac{\Delta V_{max}}{\omega L} \sin \left( \omega t - \frac{\pi}{2} \right) \quad I_{max} = \frac{\Delta V_{max}}{\omega L}$$

$$\Delta v = \Delta V_{max} \sin \omega t$$

© 2014 Thomson - Brooks/Cole


This shows that the instantaneous current  $i_L$  in the inductor and the instantaneous voltage  $\Delta v_L$  across the inductor are **out of phase** by  $(\pi / 2)$  rad =  $90^\circ$ .

# Inductors in AC circuit


$$\Delta v = \Delta V_{max} \sin \omega t$$

$$i_L = I_{max} \sin \left( \omega t - \frac{\pi}{2} \right)$$
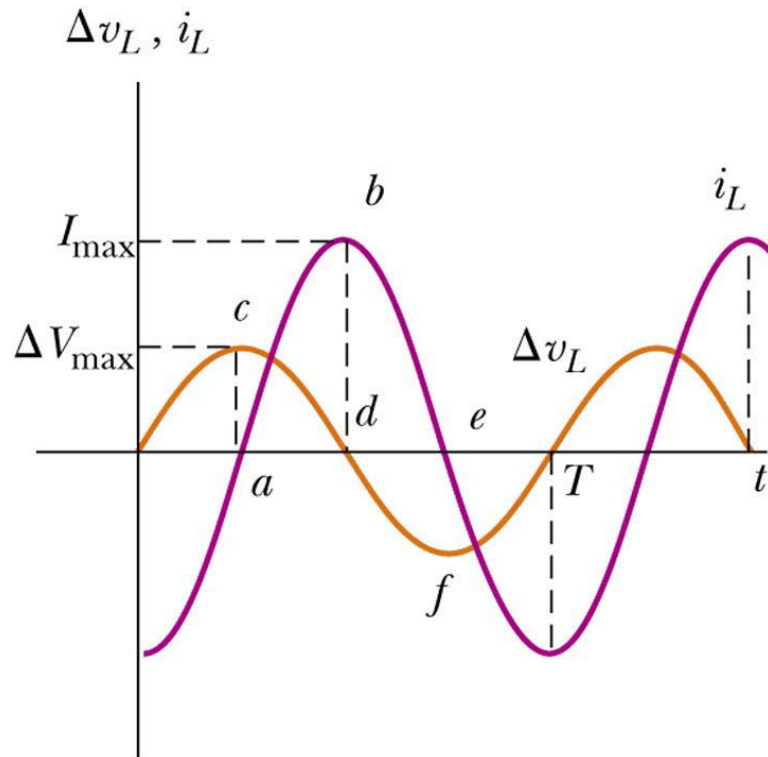
$$I_{max} = \frac{\Delta V_{max}}{\omega L}$$



© 2003 Thomson - Brooks Cole

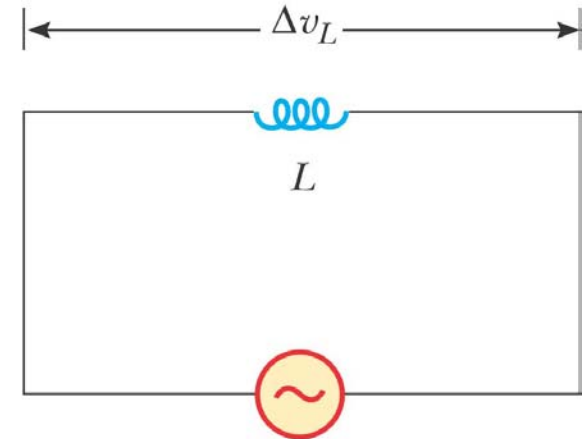

$$\Delta v = \Delta V_{max} \sin \omega t$$


©2004 Thomson - Brooks/Cole

# Inductors in AC circuit


$$\Delta v = \Delta V_{max} \sin \omega t$$

$$i_L = I_{max} \sin \left( \omega t - \frac{\pi}{2} \right)$$
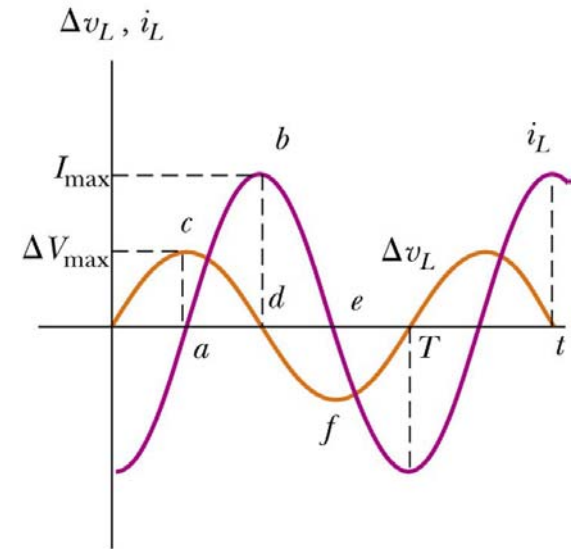
$$I_{max} = \frac{\Delta V_{max}}{\omega L}$$



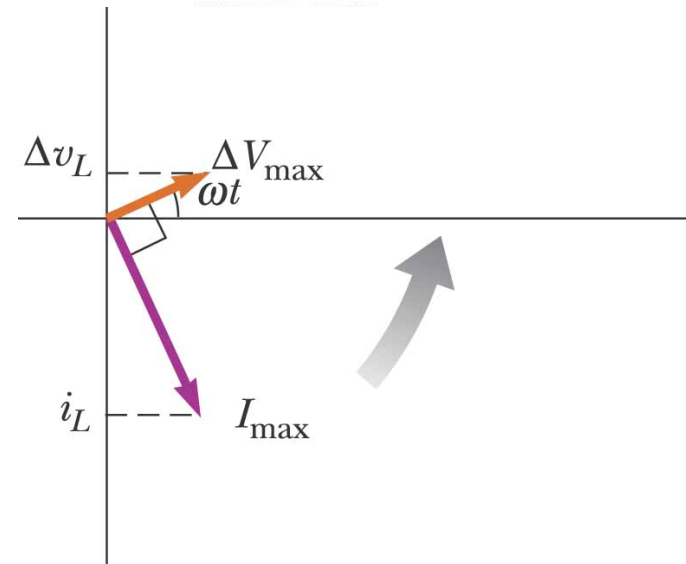- The phasors are at  $90^\circ$  with respect to each other
- This represents the phase difference between the current and voltage
- Specifically, the current lags behind the voltage by  $90^\circ$




(b)

# Inductors in AC circuit

$$\Delta v = \Delta V_{max} \sin \omega t$$

$$i_L = I_{max} \sin \left( \omega t - \frac{\pi}{2} \right)$$
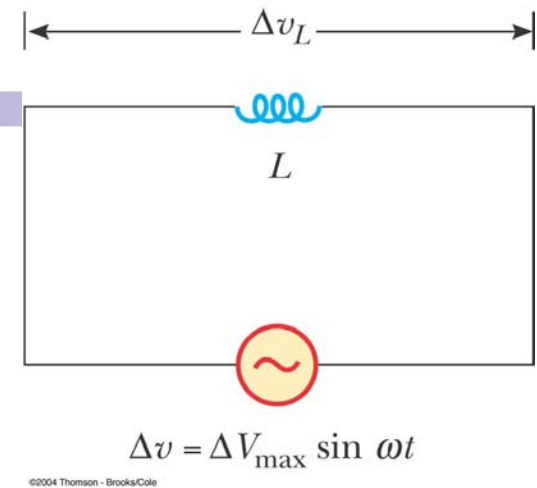
$$I_{max} = \frac{\Delta V_{max}}{\omega L}$$



- The factor  $\omega L$  has the same units as resistance and is related to current and voltage in the same way as resistance
- The factor is the **inductive reactance** and is given by:

$$X_L = \omega L$$

- As the frequency increases, the inductive reactance increases

$$I_{max} = \frac{\Delta V_{max}}{X_L}$$

# Capacitors in AC circuit

$$\Delta v + \Delta v_C = 0 \quad \text{and so}$$

$$\Delta v = \Delta v_C = \Delta V_{\max} \sin \omega t$$

- $\Delta v_C$  is the instantaneous voltage across the capacitor

- The charge is


$$q = C\Delta v_C = C\Delta V_{\max} \sin \omega t$$

- The instantaneous current is given by

$$i_C = \frac{dq}{dt} = \omega C \Delta V_{\max} \cos \omega t$$

$$i_C = \omega C \Delta V_{\max} \sin \left( \omega t + \frac{\pi}{2} \right)$$

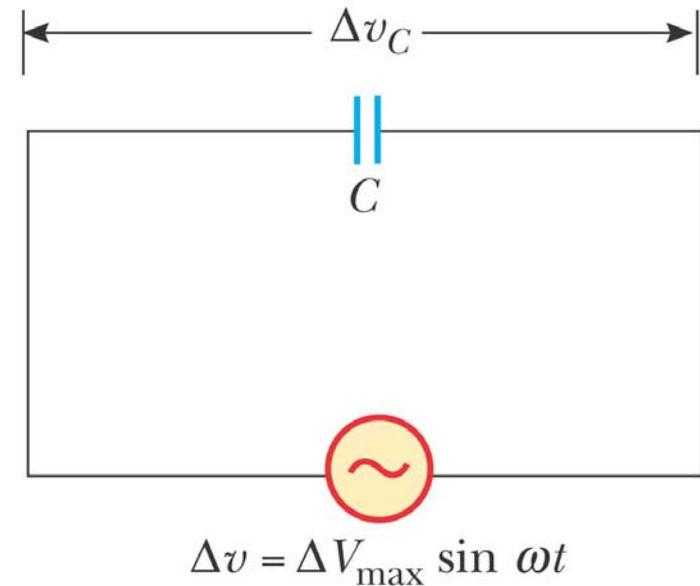- The current is  $(\pi/2)$  rad =  $90^\circ$  out of phase with the voltage




©2004 Thomson - Brooks/Cole

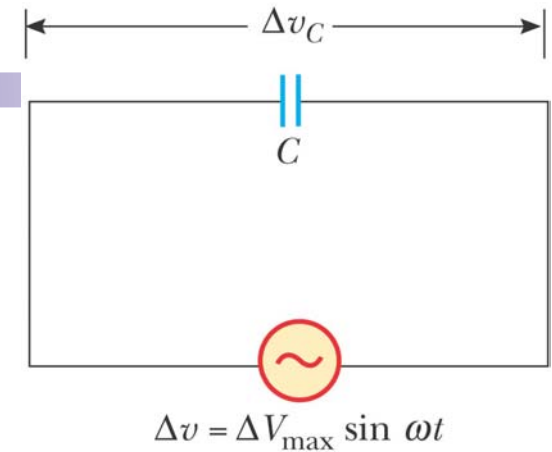
# Capacitors in AC circuit

$$\Delta v_C = \Delta V_{max} \sin \omega t$$

$$i_C = \omega C \Delta V_{max} \sin \left( \omega t + \frac{\pi}{2} \right)$$



©2004 Thomson - Brooks/Cole

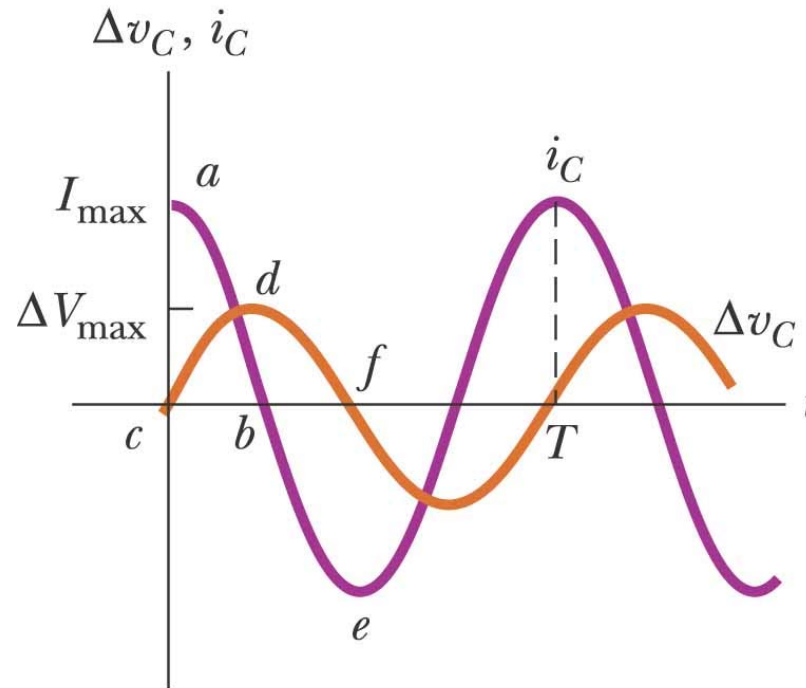

(a)


©2004 Thomson - Brooks/Cole

# Capacitors in AC circuit


$$\Delta v_C = \Delta V_{max} \sin \omega t$$

$$i_C = \omega C \Delta V_{max} \sin \left( \omega t + \frac{\pi}{2} \right)$$

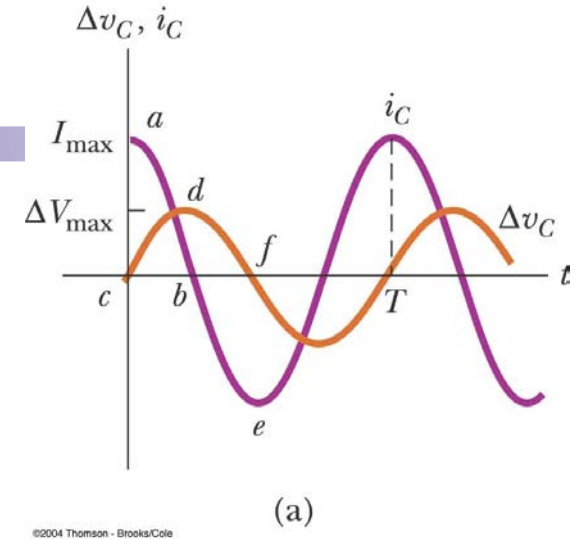- The phasor diagram shows that for a sinusoidally applied voltage, the current always leads the voltage across a capacitor by  $90^\circ$ 
  - This is equivalent to saying the voltage lags the current



©2004 Thomson - Brooks/Cole

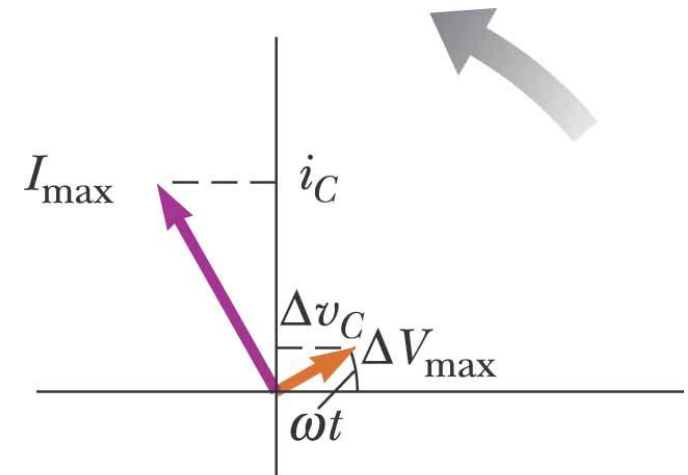

(b)


©2004 Thomson - Brooks/Cole


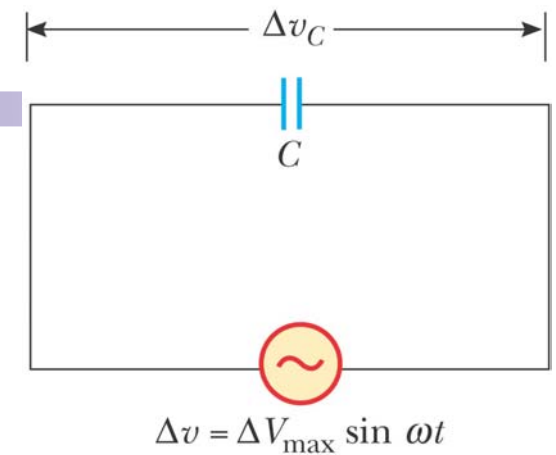
# Capacitors in AC circuit

$$\Delta v_C = \Delta V_{max} \sin \omega t$$

$$i_C = \omega C \Delta V_{max} \sin \left( \omega t + \frac{\pi}{2} \right)$$




©2004 Thomson - Brooks/Cole

- The maximum current

$$I_{max} = \omega C \Delta V_{max} = \frac{\Delta V_{max}}{(1/\omega C)}$$

- The impeding effect of a capacitor on the current in an AC circuit is called the **capacitive reactance** and is given by


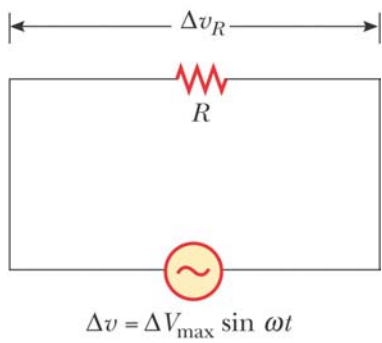
$$X_C \equiv \frac{1}{\omega C} \quad \text{and} \quad I_{max} = \frac{\Delta V_{max}}{X_C}$$



$$\Delta v = \Delta V_{\max} \sin \omega t$$

$$i_R = I_{\max} \sin \omega t$$


$$I_{\max} = \frac{\Delta V_{\max}}{R}$$

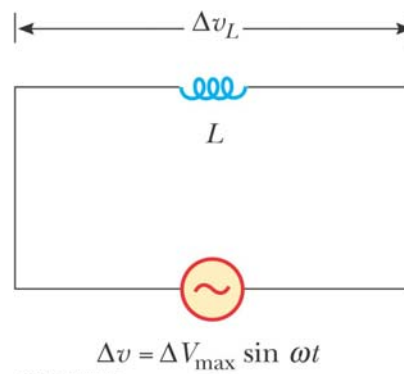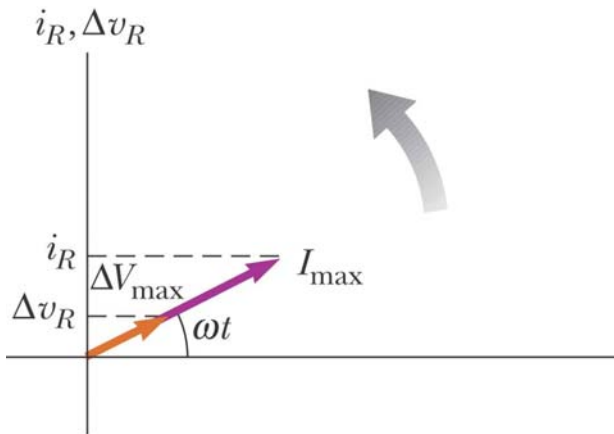


$$\Delta v = \Delta V_{\max} \sin \omega t$$

$$i_L = I_{\max} \sin \left( \omega t - \frac{\pi}{2} \right)$$
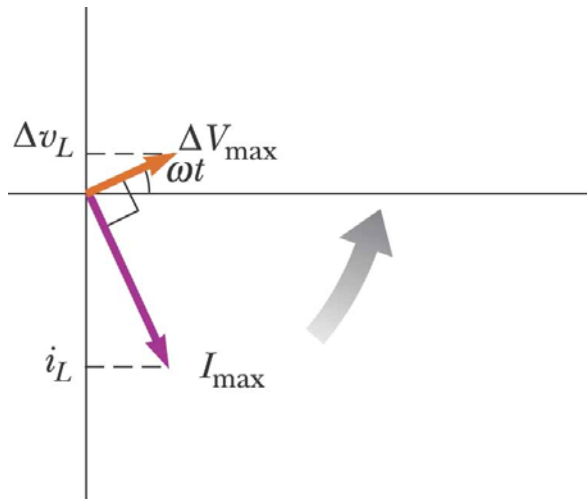
$$I_{\max} = \frac{\Delta V_{\max}}{\omega L} = \frac{\Delta V_{\max}}{X_L}$$




(b)

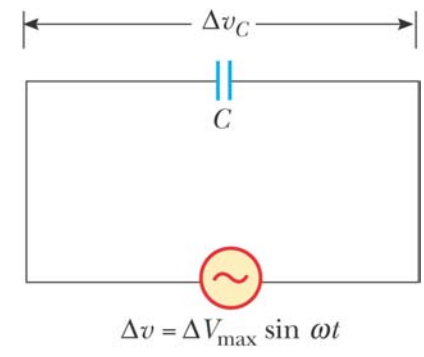

$$\Delta v_C = \Delta V_{\max} \sin \omega t$$

$$i_C = I_{\max} \sin \left( \omega t + \frac{\pi}{2} \right)$$
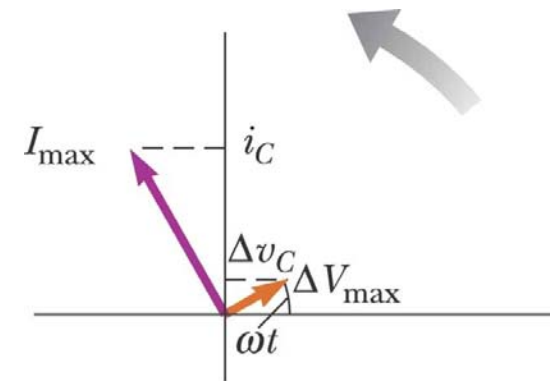
$$I_{\max} = \frac{\Delta V_{\max}}{(1/\omega C)} = \frac{\Delta V_{\max}}{X_C}$$



(b)

# RLC series circuit

- The instantaneous voltage would be given by


$$\Delta v = \Delta V_{\max} \sin \omega t$$

- The instantaneous current would be given by

$$i = I_{\max} \sin (\omega t - \varphi)$$


–  $\varphi$  is the *phase angle* between the current and the applied voltage

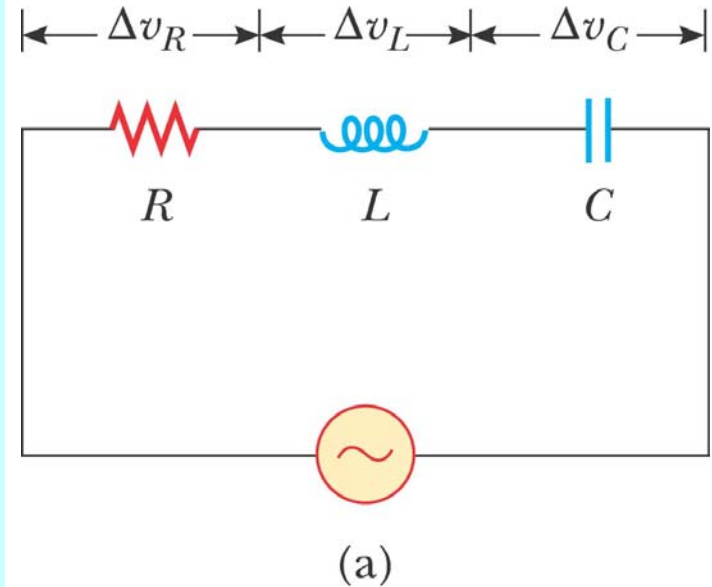- Since the elements are in series, the current at all points in the circuit has **the same amplitude and phase**




©2004 Thomson - Brooks/Cole

# RLC series circuit

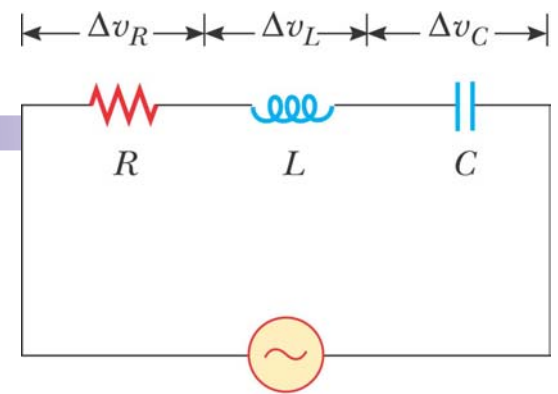


(a)

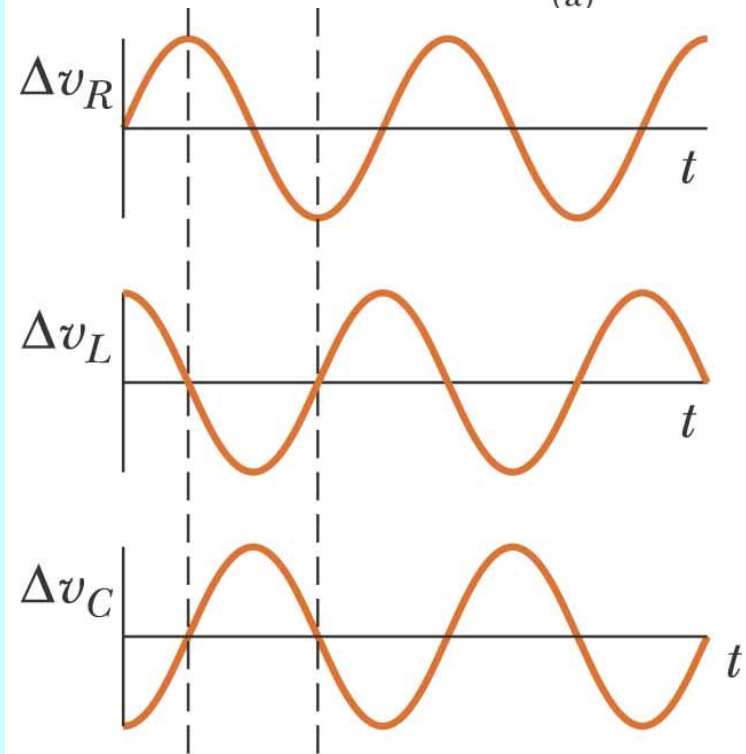- The instantaneous voltage across the resistor is in phase with the current
- The instantaneous voltage across the inductor leads the current by  $90^\circ$
- The instantaneous voltage across the capacitor lags the current by  $90^\circ$



(b)

# RLC series circuit

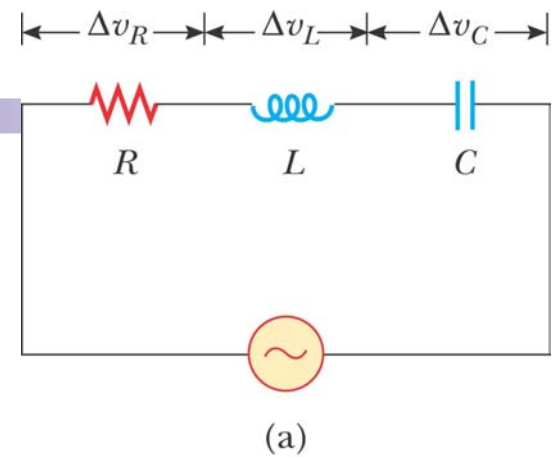


- The instantaneous voltage across each of the three circuit elements can be expressed as

$$\Delta v_R = I_{\max} R \sin \omega t = \Delta V_R \sin \omega t$$

$$\Delta v_L = I_{\max} X_L \sin\left(\omega t + \frac{\pi}{2}\right) = \Delta V_L \cos \omega t$$

$$\Delta v_C = I_{\max} X_C \sin\left(\omega t - \frac{\pi}{2}\right) = -\Delta V_C \cos \omega t$$

# RLC series circuit

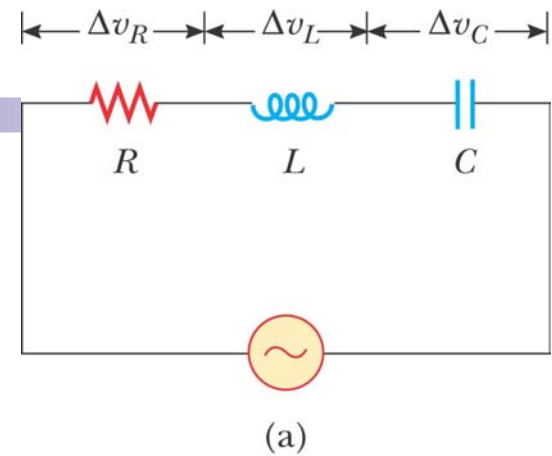

$$\Delta v_R = I_{\max} R \sin \omega t = \Delta V_R \sin \omega t$$

$$\Delta v_L = I_{\max} X_L \sin\left(\omega t + \frac{\pi}{2}\right) = \Delta V_L \cos \omega t$$

$$\Delta v_C = I_{\max} X_C \sin\left(\omega t - \frac{\pi}{2}\right) = -\Delta V_C \cos \omega t$$

- In series, **voltages add** and the instantaneous voltage across all three elements would be

$$\Delta v = \Delta v_R + \Delta v_L + \Delta v_C$$

- Easier to use the phasor diagrams

# RLC series circuit


$$i = I_{\max} \sin \omega t$$

$$\Delta v_R = I_{\max} R \sin \omega t = \Delta V_R \sin \omega t$$

$$\Delta v_L = I_{\max} X_L \sin \left( \omega t + \frac{\pi}{2} \right) = \Delta V_L \cos \omega t$$

$$\Delta v_C = I_{\max} X_C \sin \left( \omega t - \frac{\pi}{2} \right) = -\Delta V_C \cos \omega t$$

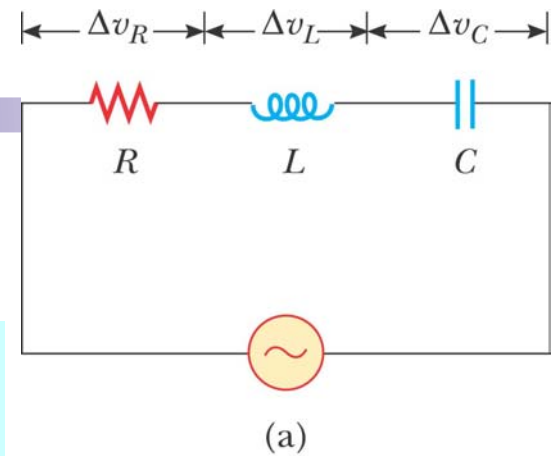
$$\begin{aligned} \Delta v &= \Delta v_R + \Delta v_L + \Delta v_C = \\ &= \Delta V_R \sin \omega t + \Delta V_L \cos \omega t - \Delta V_C \cos \omega t = \\ &= \Delta V_{\max} \sin (\omega t + \varphi) \end{aligned}$$




©2004 Thomson - Brooks/Cole

**Easier to use the phasor diagrams**


# RLC series circuit

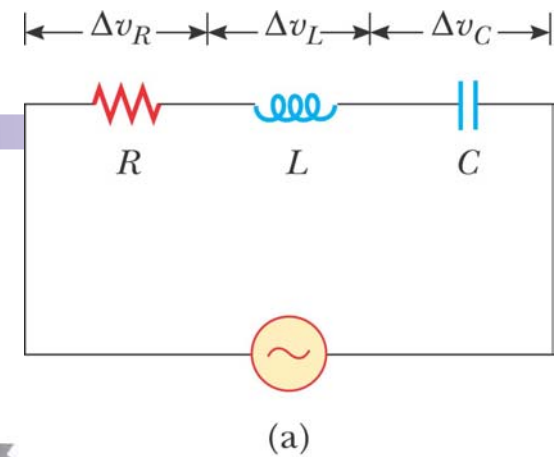


The phasors for the individual elements:

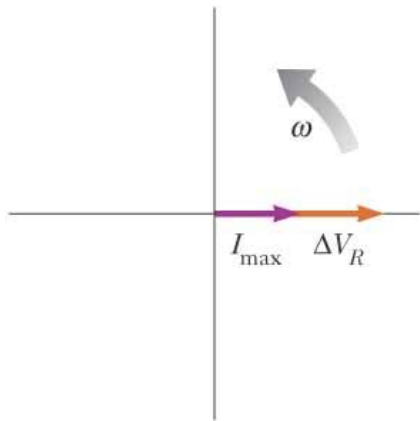

(a) Resistor

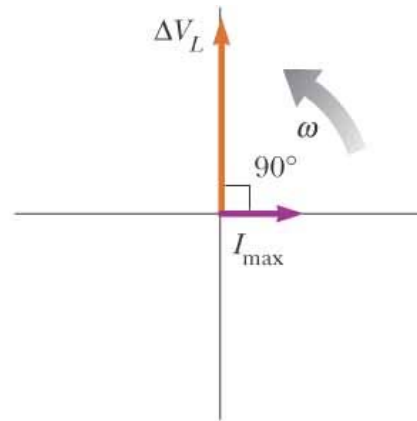


(b) Inductor

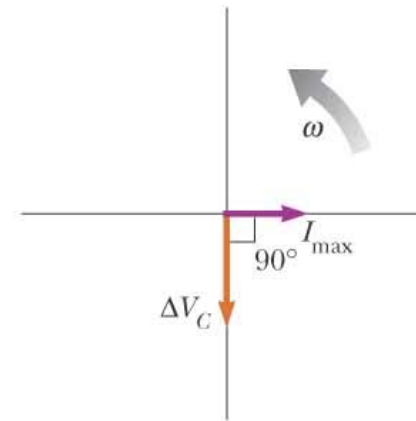

©2004 Thomson - Brooks/Cole

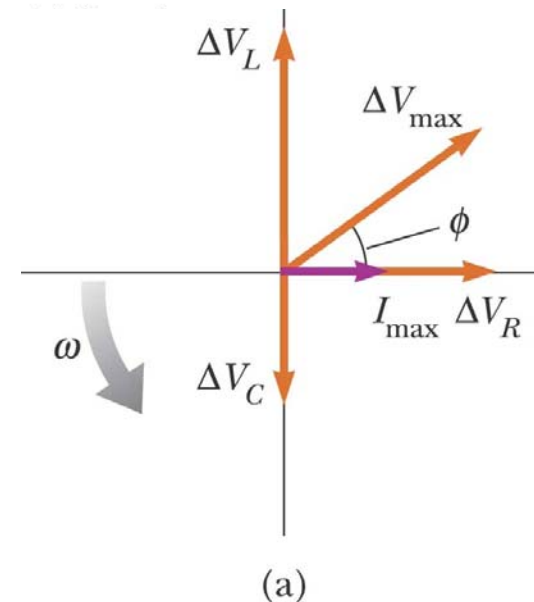- The individual phasor diagrams can be combined
- Here a single phasor  $I_{\max}$  is used to represent the current in each element
  - In series, the current is the same in each element




(a)



©2004 Thomson - Brooks/Cole



# RLC series circuit


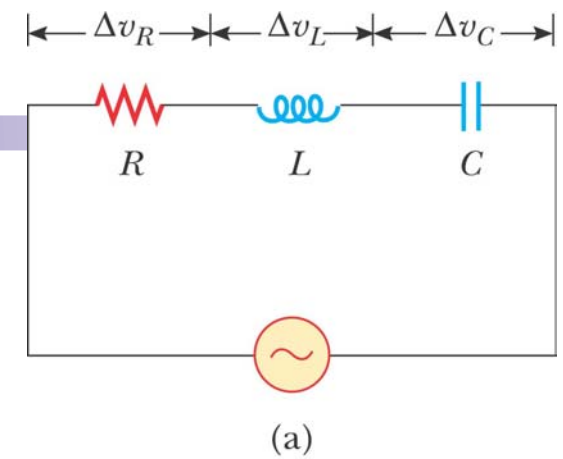


©2004 Thomson - Brooks/Cole

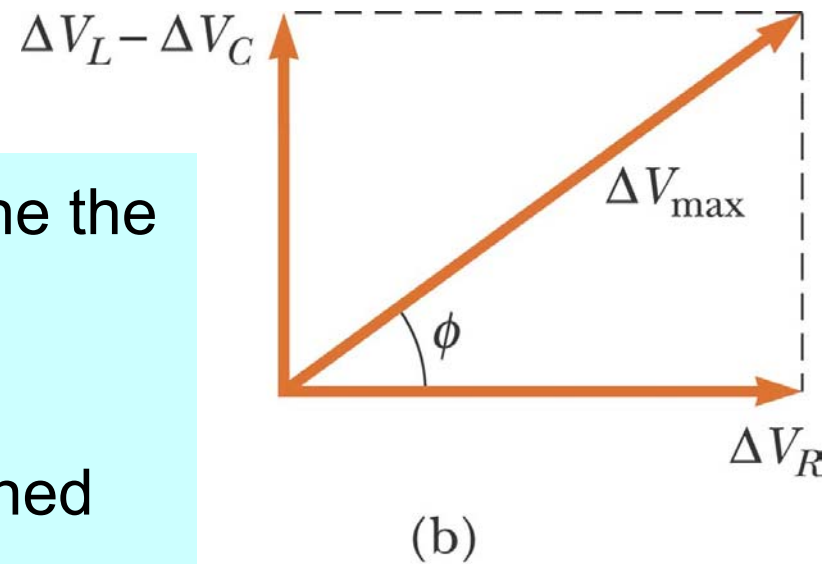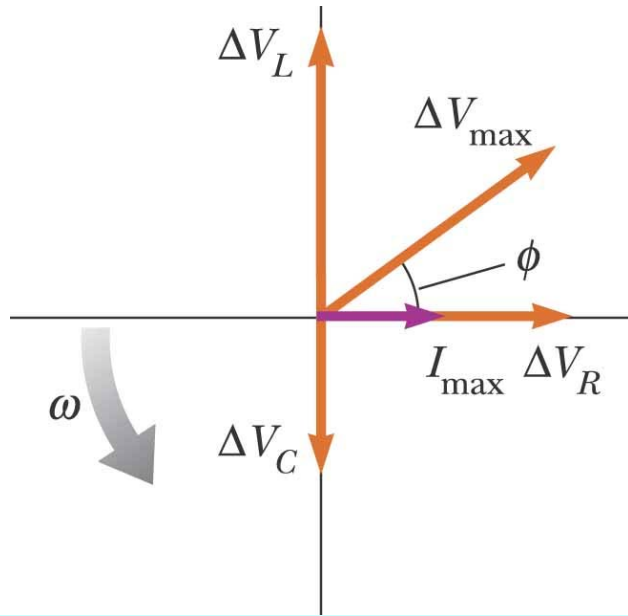

- Vector addition is used to combine the voltage phasors
- $\Delta V_L$  and  $\Delta V_C$  are in opposite directions, so they can be combined
- Their resultant is perpendicular to  $\Delta V_R$

# RLC series circuit

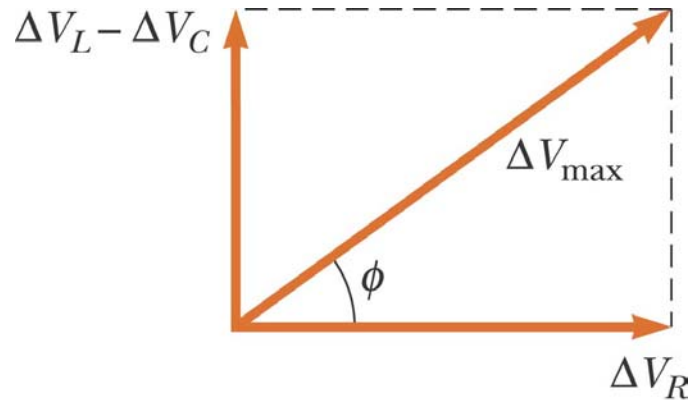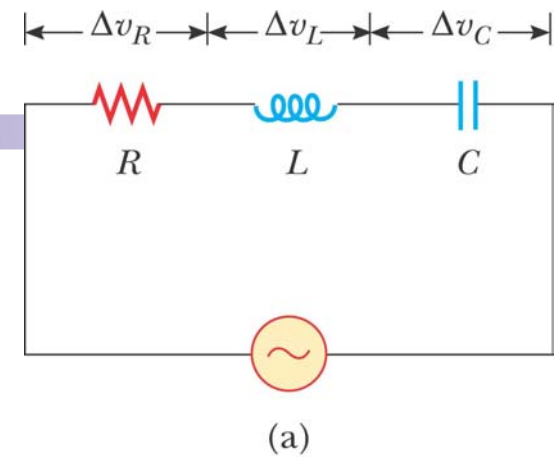


©2004 Thomson - Brooks/Cole

- From the vector diagram,  $\Delta V_{\max}$  can be calculated


$$\Delta V_{\max} = \sqrt{\Delta V_R^2 + (\Delta V_L - \Delta V_C)^2} = \sqrt{(I_{\max} R)^2 + (I_{\max} X_L - I_{\max} X_C)^2}$$

$$\Delta V_{\max} = I_{\max} \sqrt{R^2 + (X_L - X_C)^2}$$

# RLC series circuit

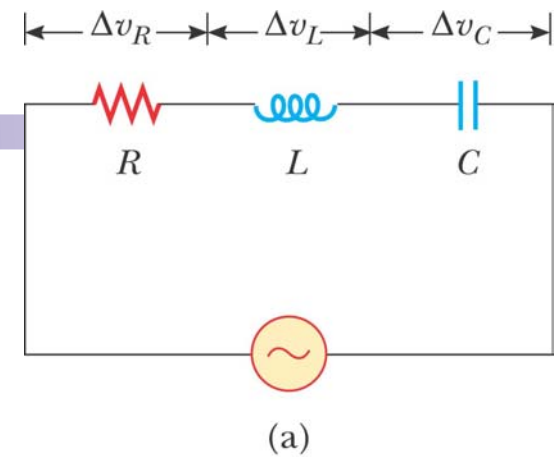

©2004 Thomson - Brooks/Cole

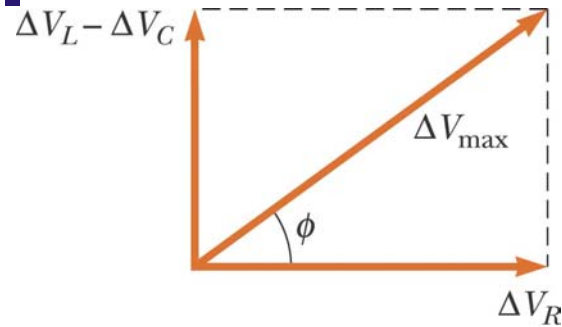

(b)

©2004 Thomson - Brooks/Cole

$$\Delta V_{\max} = I_{\max} \sqrt{R^2 + (X_L - X_C)^2}$$

- The current in an RLC circuit is

$$I_{\max} = \frac{\Delta V_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\Delta V_{\max}}{Z}$$


- **Z** is called the impedance of the circuit and it plays the role of resistance in the circuit, where

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$


# RLC series circuit

$$I_{\max} = \frac{\Delta V_{\max}}{Z}$$


$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

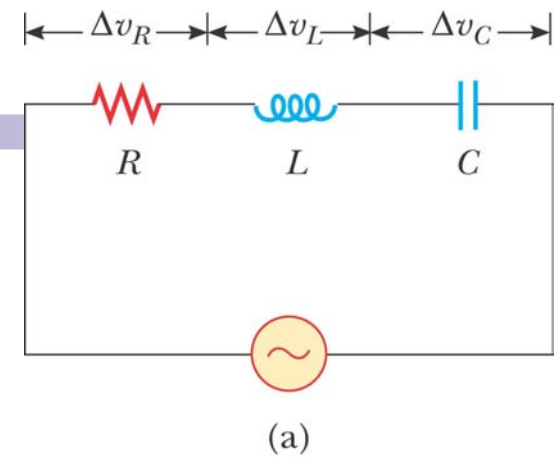


## impedance triangle

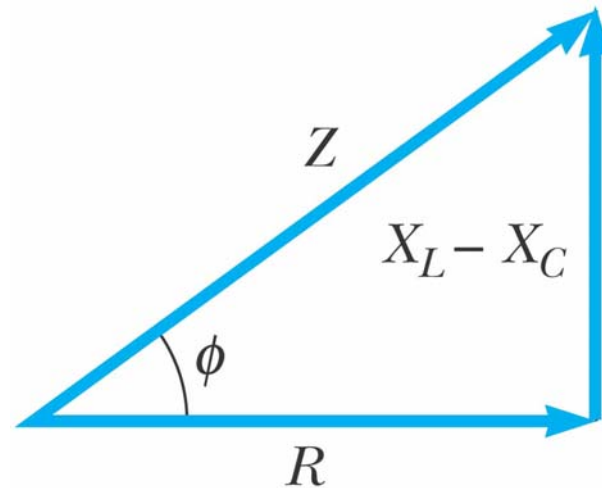

# RLC series circuit: impedance triangle

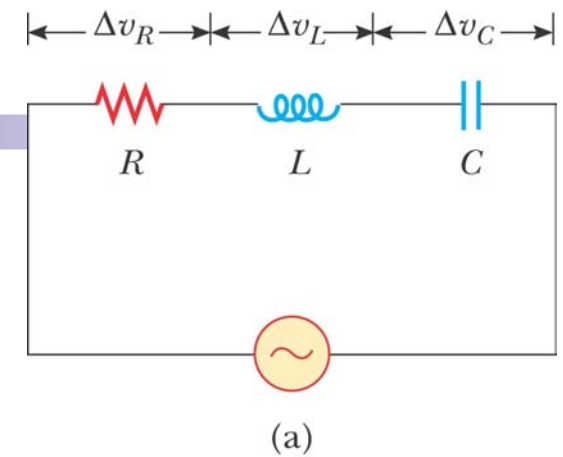

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

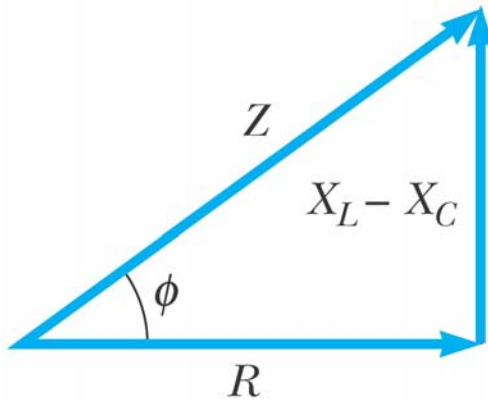

- The impedance triangle can also be used to find the phase angle,  $\phi$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

- The phase angle can be positive or negative and determines the nature of the circuit
- Also,  $\cos \phi = \frac{R}{Z}$


$$i = I_{\max} \sin \omega t$$

$$\Delta v = \Delta V_{\max} \sin (\omega t + \phi) \quad 29$$
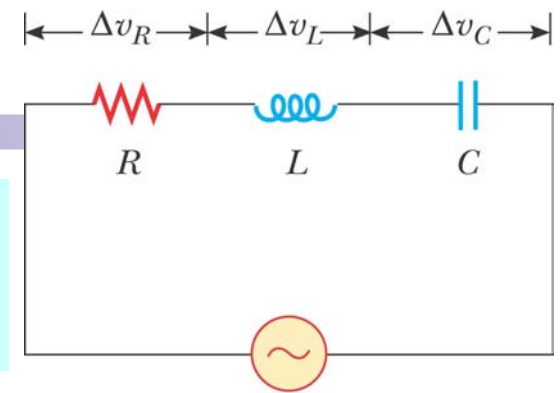
# RLC series circuit

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$




(a)

**Table 33.1**

Impedance Values and Phase Angles for Various Circuit-Element Combinations <sup>a</sup>		
Circuit Elements	Impedance $Z$	Phase Angle $\phi$
	$R$	$0^\circ$
	$X_C$	$-90^\circ$
	$X_L$	$+90^\circ$
	$\sqrt{R^2 + X_C^2}$	Negative, between $-90^\circ$ and $0^\circ$
	$\sqrt{R^2 + X_L^2}$	Positive, between $0^\circ$ and $90^\circ$
	$\sqrt{R^2 + (X_L - X_C)^2}$	Negative if $X_C > X_L$ Positive if $X_C < X_L$

<sup>a</sup> In each case, an AC voltage (not shown) is applied across the elements.

# Power in AC circuit

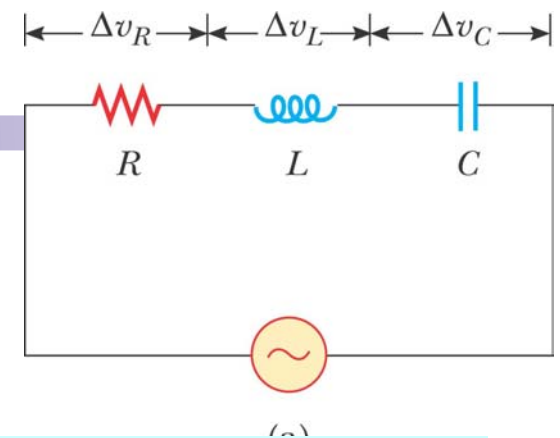

$$I_{\max} = \frac{\Delta V_{\max}}{Z}$$


$$I_{\text{rms}} = \frac{I_{\max}}{\sqrt{2}}$$

- The average power delivered by the generator is converted to internal energy in the resistor
  - $P_{\text{av}} = \frac{1}{2} I_{\max} \Delta V_{\max} \cos \varphi = I_{\text{rms}} \Delta V_{\text{rms}} \cos \varphi$
  - $\cos \varphi$  is called the *power factor* of the circuit
- We can also find the average power in terms of  $R$

$$P_{\text{av}} = I_{\text{rms}}^2 R = \frac{1}{2} I_{\max}^2 R = \frac{1}{2} \left( \frac{\Delta V_{\max}}{Z} \right)^2 R = \frac{\Delta V_{\max}^2}{2} \frac{R}{R^2 + (X_L - X_C)^2}$$
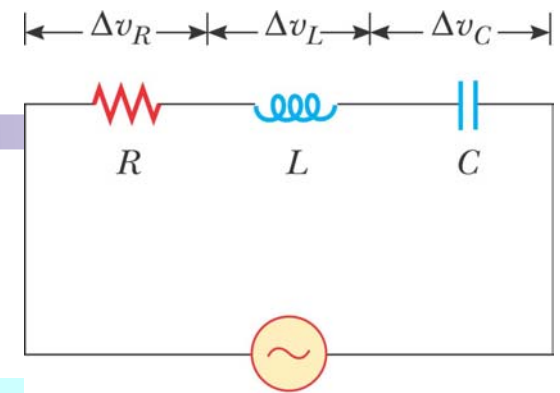
# Resonances in AC circuit

$$P_{av} = \frac{\Delta V_{max}^2}{2} \frac{R}{Z^2} = \frac{\Delta V_{max}^2}{2} \frac{R}{R^2 + (X_L - X_C)^2}$$



(a)

- Resonance in  $P_{av}(\omega)$  occurs at the frequency  $\omega_0$  where the current has its maximum value
- To achieve maximum current, the impedance must have a minimum value


– This occurs when  $X_L = X_C$  or

$$X_L = \omega_0 L = X_C = \frac{1}{\omega_0 C}$$

– Solving for the frequency gives

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

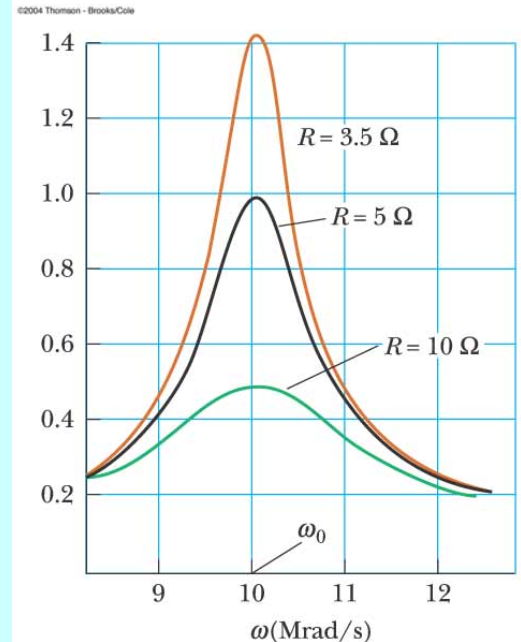- The **resonance frequency** also corresponds to the natural frequency of oscillation of an  $LC$  circuit



(a)

©2004 Thomson - Brooks/Cole




# Resonances in AC circuit

$$P_{av} = \frac{\Delta V_{max}^2}{2} \frac{R}{Z^2} = \frac{\Delta V_{max}^2}{2} \frac{R}{R^2 + (X_L - X_C)^2} = \frac{\Delta V_{max}^2}{2} \frac{R}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

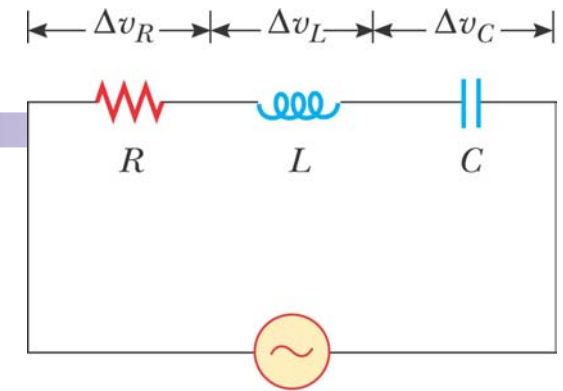
$$P_{av}(\omega_0) = \frac{\Delta V_{max}^2}{2R}$$



(a)

$L = 5.0 \mu\text{H}$   
 $C = 2.0 \text{ nF}$   
 $\Delta V_{\text{rms}} = 5.0 \text{ mV}$   
 $\omega_0 = 1.0 \times 10^7 \text{ rad/s}$

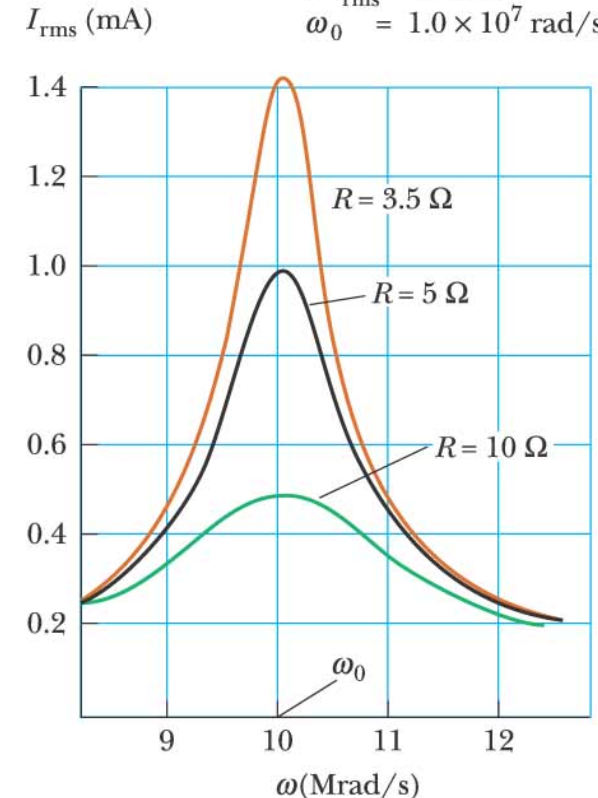- Resonance occurs at the same frequency regardless of the value of **R**
- As **R** decreases, the curve becomes narrower and taller
- Theoretically, if **R = 0** the current would be infinite at resonance
  - Real circuits always have some resistance



(a)